



INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

LOGIC GATES

WHAT IS A LOGIC GATE?

- Digital Computers that we know and love contain transistors, that act as a switch
- Each switch has an on or off position
- Computer scientists represent this position of on and off as 1 and 0
- This is the language that computers speak which is represented as binary

WHAT IS A LOGIC GATE?

- If you recall back to the first week we talked about bits nibbles and bytes. An individual bit can either be 1 or 0
- Computers don't just store the data that is going into each bit, it is also being processed
- Information is processed from an input into an output



INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

WHAT IS A LOGIC GATE?

- Logic gates are what we use to process our data
- They take inputs and produce outputs depending on the rules or logic that is used
- Logic gates are both abstract concepts and real processes that allow computer systems to make “decisions”



INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

WHAT IS A LOGIC GATE?

- The basic logic gates include:
- AND
- OR
- NOT
- NAND
- NOR
- XOR
- XNOR



INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

WHAT IS A LOGIC GATE?

- https://www.youtube.com/watch?v=zcsmHkKJgbE&ab_channel=3DSage




INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

AND GATE

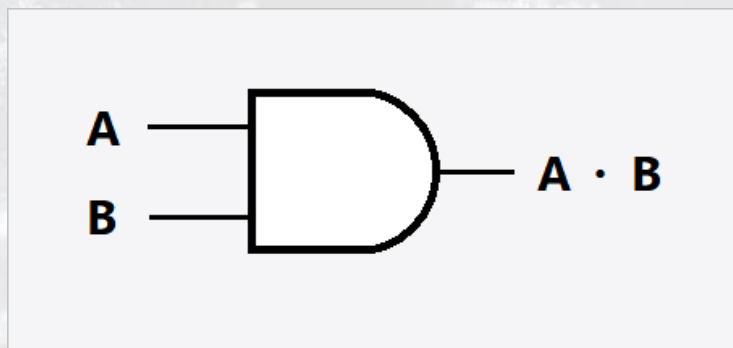- AND gates have two inputs. Both inputs must be a 1 (1,1) for us to output a 1. All other inputs (1,0) or (0,1) or (0,0) will output a 0






INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

OR GATE

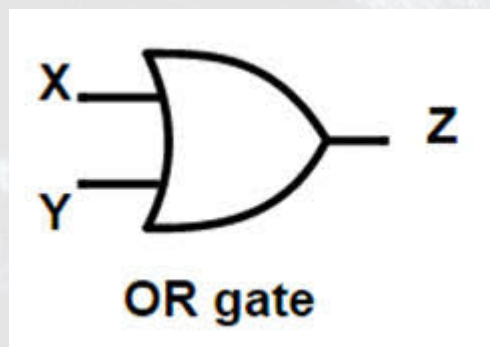- OR gates have two inputs. Unlike the AND gates OR gates can have (1,0) or (0,1) or (1, 1) as inputs and output a 1. The only input that will output a 0 is (0,0)






INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

XOR GATE (EXCLUSIVE OR)

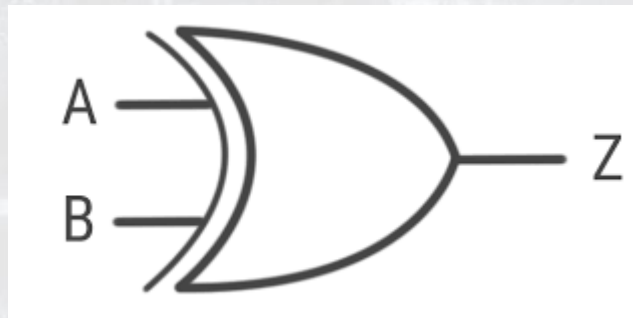- XOR gates output a 1 only when there the logic is (1,0) or (0,1). All others (0,0) and (1,1) will output a 0






INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA


NOT GATE

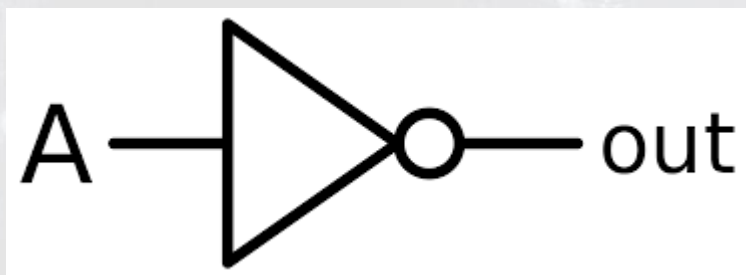- NOT gates have one input and one output. Not gates work by outputting the opposite of what is input. If there is a 1 input, the output will be 0. if there is a 0 input then it inverts it and outputs a 1



NAND GATE

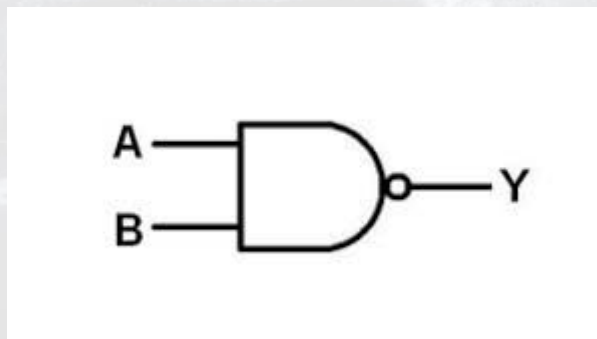- NAND gates invert AND gates. NAND gates will take in (1,1) then will invert it to a 0. When there is any other input (1,0) and (0,1) and (0, 0) it will output a 1






INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

NOR GATE

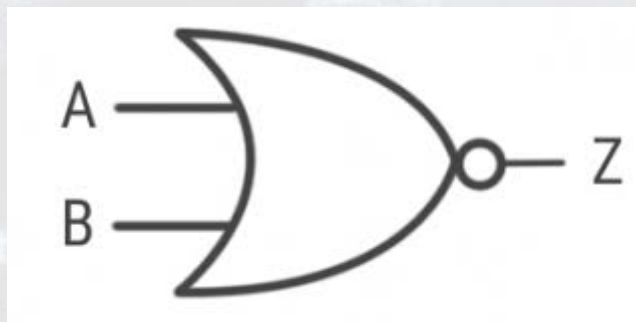- NOR gates invert OR gates. Input (1,0) or (0,1) or (1,1) the output will be 0. The only Input that will output a 1 is (0,0)







INSTITUTE OF
TECHNOLOGY
DEVELOPMENT
OF CANADA

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

XNOR GATE

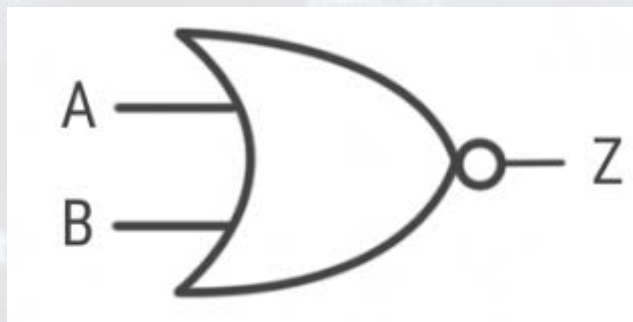- XNOR gates invert NOR gates. Input (1,0) or (0,1) the output will be 0. Input (0,0) or (1,1) and the output will be 1. this is exclusively not or



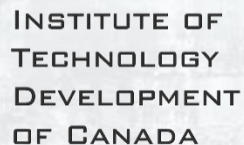

475 GRANVILLE STREET, VANCOUVER, BC, V6C 1T1
PHONE: +1(604)558-8727, +1(604)409-8200
TOLL FREE: +1(888) 880-4410
FAX: +1(888) 881-6545
WEB: WWW.ITDCANADA.CA
EMAIL: STUDYING@ITDCANADA.CA

